

Design of Closed Loop Boost Converter

EE 561

Sambit Panda(214102114)

Sanjay Kumar Sahu(214102115)

November 14,2021

1 Objective

To realize the closed loop control of boost converter using analogue PI controller


2 Software

LT Spice & Eagle PCB

3 Introduction

A DC-DC converter is a circuit which converts a constant dc supply to a variable dc supply. In closed loop control the output voltage is compared with the required voltage reference and the error signal is supplied to PI controller which is designed in analogue domain. Then the output of the PI controller is compared with the output of triangular wave generator designed in analogue domain . The error produced is provided to the MOSFET gate driver IC which produces required pulse waveform for the switch. A snubber is used to protect the gate terminal of the switch. In order to change the output voltage we need to change the reference so that new gate pulse will be generated as per our requirement.

4 Circuit Diagram

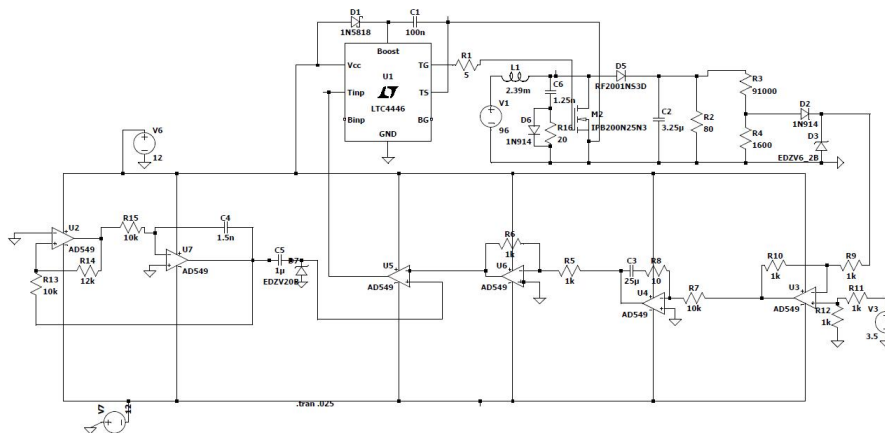

5 Design

$$P = 500w, V_{in} = 96v, V_o = 200v, f_s = 20kHz$$

$$\text{percentage } \nabla V_o = 10, \text{percentage } \nabla I_L = 20$$

$$R_0 = 200^2/500 = 80\Omega, V_o/V_{in} = 1/(1-D), D = 0.52$$

$$\nabla I_L/I_o = D(1-D)^2 R/Lf_s \text{ hence } L = 2.39mH$$

$$\nabla V_o/V_o = D/Rf_s C \text{ hence } C = 3.25 * 10^{-6}F$$

$$V_{ref} = 200(1.6/91 + 1.6) = 3.5v, I_o = 500/200 = 2.5A, I_{in} = 500/96 = 5.2A$$

$$\text{Open loop tf} = \frac{V_o R(1-D)^2 - V_o S L}{S L(1-D) + S^2 L C R(1-D) + (1-D)^3 R} = \frac{12.32 * 10^9 (1 - 1.3 * 10^{-4} S)}{S^2 + 3846.15 S + 29.58 * 10^6}$$

$$\text{Closed loop tf} = \frac{12.32 * 10^9 (1 - 1.3 * 10^{-4} S)}{S^2 + 3846.15 S + 29.58 * 10^6} (K_p + \frac{K_i}{S})$$



Lets assume $W_{gc} = 5kHz$ and phase margin = 30°

Then $K_p = 0.0010246$ and $K_i = 4.356$

$$(K_p + \frac{K_i}{S}) = (\frac{R_8}{R_7} + \frac{1}{S R_7 C_3})$$

If $R_7 = 10k\Omega$ then $R_8 = 10.246\Omega$ and $C_3 = 25 * 10^{-6}F$

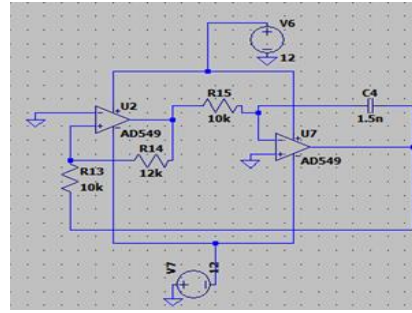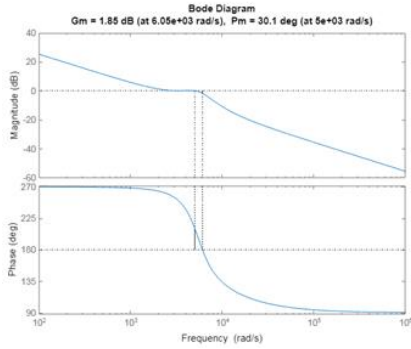Peak voltage of triangular wave = $V_{sat}(R_{13}/R_{14}) = 10v$



Peak voltage of triangular wave(after level shift) = $20v$

$$\text{Frequency} = R_{14}/4R_{13}C_4R_{15} = 12k/(4 * 10k * 10k * 1.5n) = 20kHz$$

$$\text{In snubber circuit } R = V_{sw}/I_{max} = 200/10 = 20 \text{ and } C = 1/(v^2 f) = 1.25nF$$

6 Components

1. Voltage sources: 96v(input), 12v(opamp), 3.5v(reference)

2. Opamp: AD549(LTSpice)/LM324AN-NOPB(Eagle)

3. Mosfet: max. voltage = 200v, volt. rating = $1.5 * 200 = 300v$

max. current = $5.2 + 5.2 * 0.1 = 5.72A$

Model: IPB200N25N3(LTSpice)/IRF644(Eagle)

4. Diode: max. voltage = $200 - 96v = 104$, volt. rating = $1.5 * 104 = 156v$

max current = $2.5 + 2.5 * 0.1 = 2.75A$

Model: RF2001NS3D(LTSpice)/BY550(Eagle)









5. Scaling circuit diode: EDZV6-2B(LTSpice)/1N5333(Eagle)

6. Gate driver: LTC4446





7. Snubber circuit diode: 1N914(LTSpice)/BY550(Eagle)

8. Tri. wave generator diode: EDZV20B(LTSpice)/1N4004(Eagle)

7 Waveforms

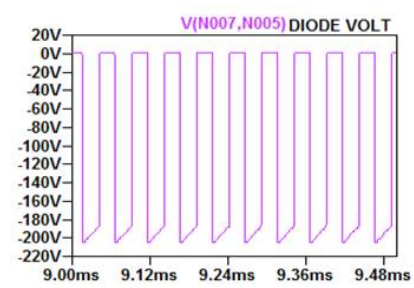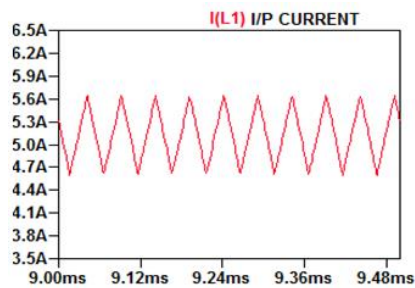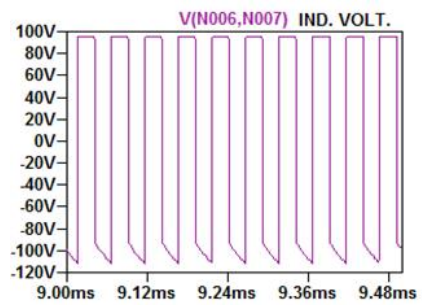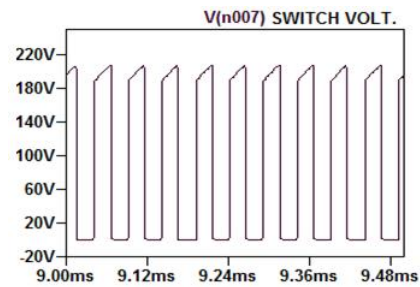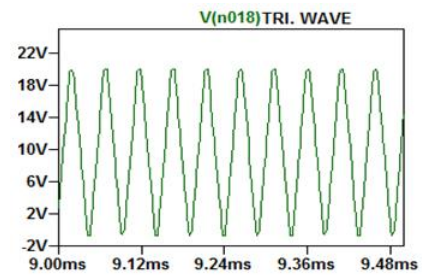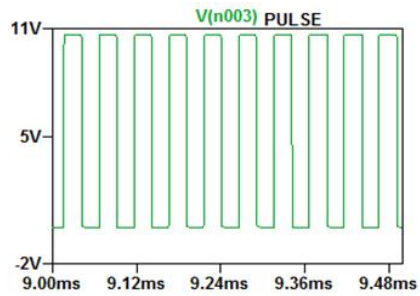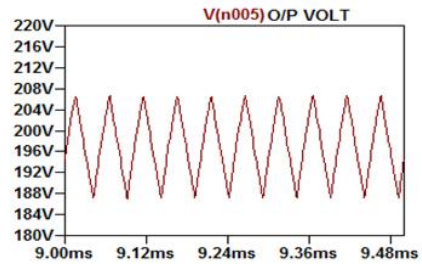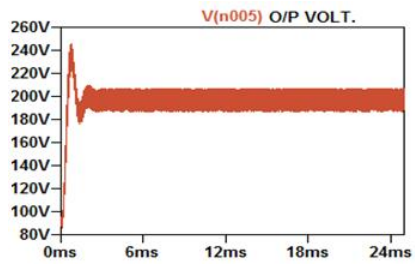

8 Eagle Schematic and PCB Layout

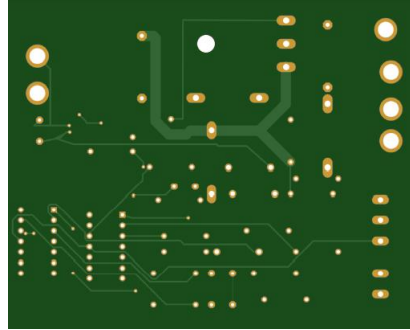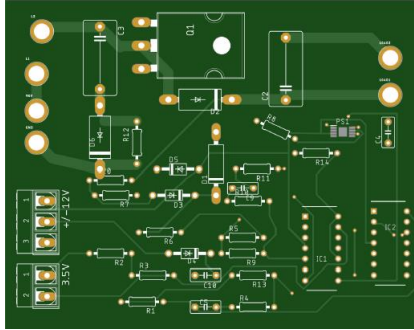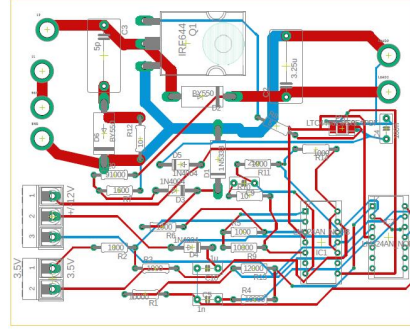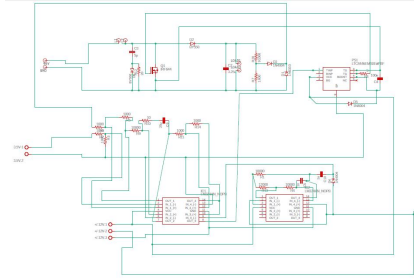

9 Conclusion

In this project we observed the closed loop control of boost converter using analog PI controller. From LT Spice simulation the average output voltage is found to be 196v. The ripple in output voltage is 18v. The average inductor/input current is 5.2A and the ripple in inductor current is 1A. The average load current is found to be 2.45A. The converter is working in continuously conduction mode. And the PCB board is designed in EAGLE PCB with choosing appropriate ratings both in LTSpice and Eagle PCB.